

Resistance and Ohm's Law

SPH4C


Resistance is the property of substances that _____ the free flow of electrons.

It is measured in units of _____ (_____).

_____ such as lights and heating elements have a resistance: they impede the flow of electrons and _____ the energy of the electrons into another form of energy such as _____ or _____.

A _____ is a load placed in a circuit simply to impede the flow of electrons and thus _____ to the rest of the circuit.

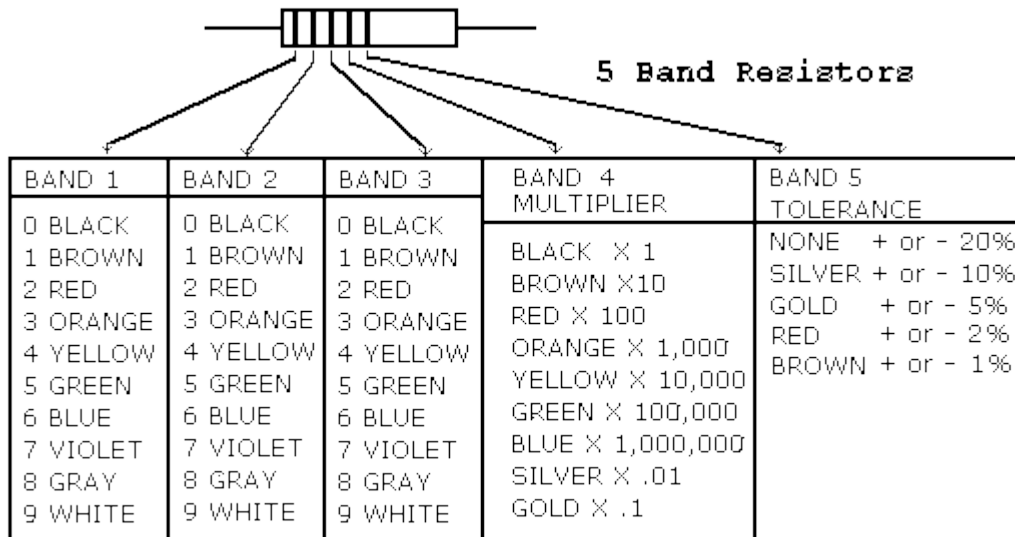The resistance of a resistor is typically indicated by _____:



Example: Yellow - Violet - BLACK - BLACK - Brown
 4 + 7 + 0 × 1 = 470 Ohms 1% Tolerance

The current that flows through a resistor will be equal to:

This is called Ohm's Law and is often written:

Example:

If a 50-Ω resistor is connected to a 1.5 V battery, what is the current through the resistor?

More Practice

1. Match each term on the left to the most appropriate description of the term on the right.

- | | |
|----------------------------|--|
| _____ circuit | A. a measure of the opposition to current flow |
| _____ current | B. the energy stored per coulomb of charge in a circuit |
| _____ load | C. the rate of flow of charge |
| _____ potential difference | D. the path of electric current flow |
| _____ resistance | E. a device that converts electric energy to other forms |

2. To measure the current through a component, an ammeter should be connected:

- A. in series B. in parallel
C. either A or B D. neither A nor B

3. To measure the potential difference across a component, a voltmeter should be connected:

- A. in series B. in parallel
C. either A or B D. neither A nor B

4. A student connects a $5\ \Omega$ resistor to a 10 V power supply. What will be the current in the circuit?

- A. 0.5 A B. 2 A C. 50 A D. 250 A

5. If the resistance in a circuit is decreased, the potential difference supplied to the circuit will:

- A. increase B. decrease C. remain the same

6. What is the resistance of each of the following 5-band resistors?

(A) Orange – Blue – Black – Black – Gold

(B) Red – Violet – Green – Orange – Silver

(C) Brown – White – Red – Black – Brown