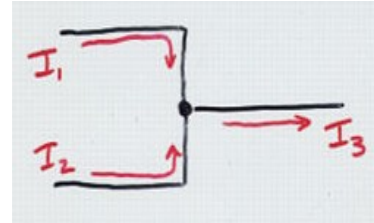


Kirchoff's Laws for Circuit Analysis

SPH4C


At any junction point in an electrical circuit,

the _____ the junction equals the _____ the junction.



In any complete path in an electrical circuit,

the _____ equals the _____.

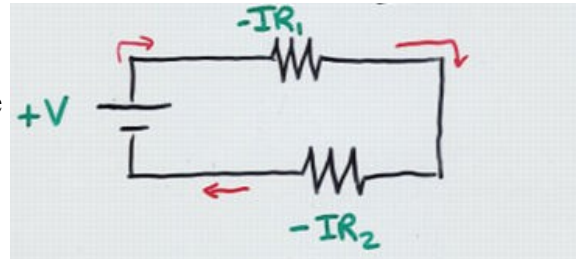

The Laws for a Series Circuit

The current is _____ at all points in the circuit:

The total voltage supplied to the circuit is equal to the sum of the voltage drops across the individual loads:

$$V_T = V_1 + V_2 + \dots$$

Given this, from Ohm's Law, $V = IR$


$$I_T R_T = I_1 R_1 + I_2 R_2 + \dots$$

Since $I_T = I_1 = I_2 = \dots = I$,

$$I R_T = I R_1 + I R_2 + \dots$$

Divide all terms by I and the equivalent resistance is the _____ :

Example:

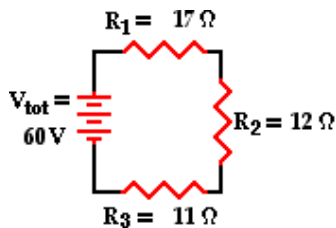

$R_{eq} =$ Ω $I_{tot} =$ A


$I_1 =$ A $V_1 =$ V

$I_2 =$ A $V_2 =$ V

$I_3 =$ A $V_3 =$ V

The Laws for a Parallel Circuit

At a junction:

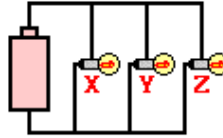

$$I_T = I_1 + I_2 = \dots$$

But the total voltage across each of the branches is _____:

Given $I_T = I_1 + I_2 + \dots$

From Ohm's Law, $V = IR$ or $I = V/R$


$$V_T/R_T = V_1/R_1 + V_2/R_2 + \dots$$

Since $V_T = V_1 = V_2 = \dots = V$


$$V/R_T = V/R_1 + V/R_2 + \dots$$

Divide all terms by V and the _____ of equivalent resistance is the sum of the _____ of the individual resistances:

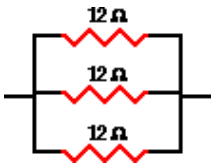
Example: Find the equivalent resistance of



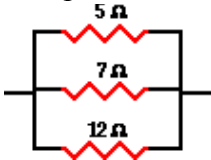Example: Find the equivalent resistance of



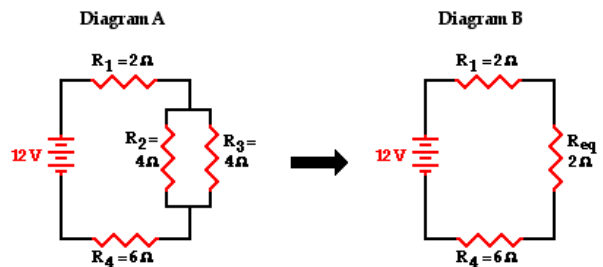What do we do if a circuit has both series and parallel loads? Find the equivalent resistance of the loads in parallel and continue the analysis.



More Practice

Match each of the configurations of resistors on the left to their equivalent resistance on the right.

- | | |
|--|---------------|
| _____ two 12Ω resistors in series | A. 2Ω |
| _____ two 12Ω resistors in parallel | B. 4Ω |
| _____ a 12Ω resistor and 6Ω resistor in series | C. 6Ω |
| _____ a 12Ω resistor and 6Ω resistor in parallel | D. 18Ω |
| _____ 12Ω , 6Ω , and 4Ω resistors in series | E. 22Ω |
| _____ 12Ω , 6Ω , and 4Ω resistors in parallel | F. 24Ω |

- 60 V is supplied to a circuit with a $10\text{-}\Omega$ resistor and a $20\text{-}\Omega$ resistor in parallel. The voltage drop across the resistors is:
 - 10 V across the $10\text{-}\Omega$ resistor and 20 V across the $20\text{-}\Omega$ resistor
 - 20 V across the $10\text{-}\Omega$ resistor and 40 V across the $20\text{-}\Omega$ resistor
 - 30 V across each resistor
 - 60 V across each resistor
- In the previous question, if I_{10} is the current across the $10\text{-}\Omega$ resistor and I_{20} is the current across the $20\text{-}\Omega$ resistor, which of the following is true?
 - $I_{10} < I_{20}$
 - $I_{10} > I_{20}$
 - $I_{10} = I_{20}$
 - It cannot be determined.
- 60 V is supplied to a circuit with a $10\text{-}\Omega$ resistor and a $20\text{-}\Omega$ resistor in series. The voltage drop across the resistors is:
 - 10 V across the $10\text{-}\Omega$ resistor and 20 V across the $20\text{-}\Omega$ resistor
 - 20 V across the $10\text{-}\Omega$ resistor and 40 V across the $20\text{-}\Omega$ resistor
 - 30 V across each resistor
 - 60 V across each resistor
- In the previous question, if I_{10} is the current across the $10\text{-}\Omega$ resistor and I_{20} is the current across the $20\text{-}\Omega$ resistor, which of the following is true?
 - $I_{10} < I_{20}$
 - $I_{10} > I_{20}$
 - $I_{10} = I_{20}$
 - It cannot be determined.
- Is the total current around the circuit greater in Question 1 or in Question 3?
 - Question 1
 - Question 3
 - It's the same.
 - It cannot be determined.