


# Other Circuit Components

## SPH4C

**Semi-conducting materials** exhibit \_\_\_\_\_ properties. The way in which the material is connected to a power supply determines whether it will conduct an electrical current or impede it from flowing.

The most common semi-conducting material is \_\_\_\_\_, which needs to have very small amounts of other elements such as boron and phosphorous added to it in order to become a semi-conductor. This is called \_\_\_\_\_.

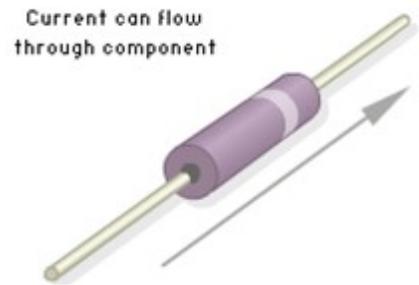The simplest kind of semiconductor device is a \_\_\_\_\_, in which the electrical current can be made to flow in \_\_\_\_\_ direction only. If the diode is reversed the flow of current is prevented. The direction that current is allowed to pass is called the \_\_\_\_\_.



The direction that current is not allowed to pass is called the \_\_\_\_\_.


A common use for diodes is in \_\_\_\_\_ circuits, which changes alternating current (AC) into \_\_\_\_\_ current (DC), as in a cell phone charger.

A **light-emitting diode** or \_\_\_\_\_ is a special kind of diode, made from gallium arsenide phosphide, that \_\_\_\_\_ when current passes through it (an ILED emits \_\_\_\_\_ light). The current required to power an LED is usually \_\_\_\_\_.

\_\_\_\_\_ on a **photodiode** generates an electrical current (in photovoltaic mode). Photodiodes are the basis of \_\_\_\_\_.

**Transistors** have three leads: the \_\_\_\_\_, \_\_\_\_\_ and \_\_\_\_\_.

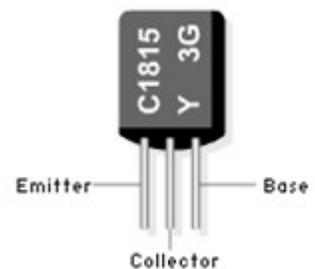A \_\_\_\_\_ current at the \_\_\_\_\_ terminal (that is, flowing from the base to the emitter) can \_\_\_\_\_ or \_\_\_\_\_ a much \_\_\_\_\_ current between the \_\_\_\_\_ and emitter terminals.



A **capacitor** is a discrete component which can \_\_\_\_\_  
 an electrical \_\_\_\_\_ for a period of time. The larger  
 the \_\_\_\_\_ the more charge it can store.




When you **connect a capacitor to a battery**, here's what happens:

The \_\_\_\_\_ on the capacitor that attaches to the \_\_\_\_\_ terminal of the battery \_\_\_\_\_ electrons that the battery is producing.

The plate on the capacitor that attaches to the positive terminal of the battery \_\_\_\_\_ electrons to the battery.

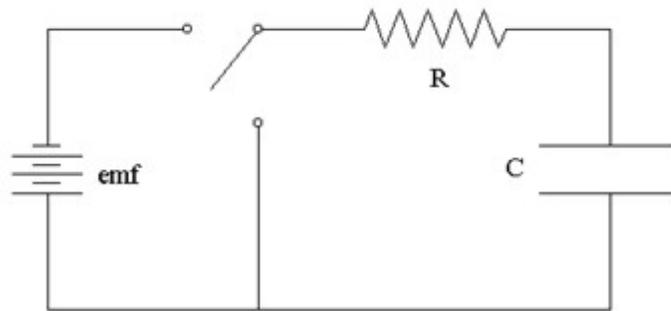Once it's charged, the capacitor has the \_\_\_\_\_ as the battery.



Here you have a battery, a light bulb and a capacitor.

When you closed the switch to connect the battery, the light bulb would \_\_\_\_\_ as current flows from the battery to the capacitor to \_\_\_\_\_. The bulb would get \_\_\_\_\_ and finally go out once the capacitor \_\_\_\_\_.

Then you could change the switch position. Current would flow from one plate of the capacitor to the other. The light bulb would light and then get dimmer and dimmer, finally going out once the capacitor had completely \_\_\_\_\_ (the same number of electrons on both plates). The difference between a capacitor and a battery is that a capacitor can \_\_\_\_\_ its entire charge in a tiny fraction of a second. The electronic \_\_\_\_\_ on a camera uses a capacitor